

# Thapar University, Patiala


## DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Course Code: UEC 301; Course Name: Analog Electronics

B. Tech, ECE (III-Sem), "Tutorial Sheet No. - 3"

### Solution

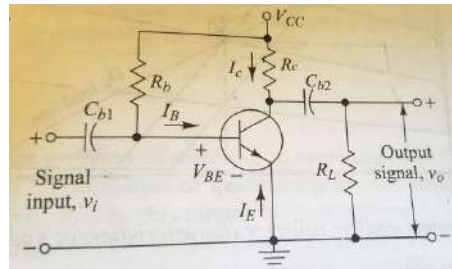**Q.1** In the circuit of Fig.1, let  $V_{CC} = 5\text{ V}$ ,  $R_b = 430\text{ k}\Omega$ , and  $R_c = 2.5\text{ k}\Omega$ . If  $V_{BE} = 0.7$ , then determine the dc voltage at the collector for  $\beta = 100, 150$ , and  $200$ .



$$I_B = \frac{V_{CC} - V_{BE}}{R_b} = I_{B2} \approx \frac{V_{CC}}{R_b}$$

*Solution* With  $V_{BE} = 0.7\text{ V}$ , from Eq. (9.1),

$$I_B = \frac{(5 - 0.7)}{430\text{ K}} = 10\text{ }\mu\text{A}$$

Assuming the transistor to be in the active mode,

$$I_C = \beta I_B$$

and

$$V_C = V_{CC} - R_c I_C = 5 - 0.025\beta$$


Hence, for  $\beta = 100, 150$  and  $200$ , we get, respectively,

$$V_C = 2.5\text{ V}, 1.25\text{ V and } 0\text{ V.}$$

Clearly, for  $\beta = 100$  and  $150$ , the transistor is in the active mode, while for  $\beta = 200$ , the transistor has gone into saturation, in which case,  $V_C$  will be  $0.2\text{ V}$ .

This example illustrates that variations in  $\beta$  (due to process variations) can cause a fixed-bias circuit to go out of the active mode of operation, if  $\beta$  becomes too high compared to its nominal value.

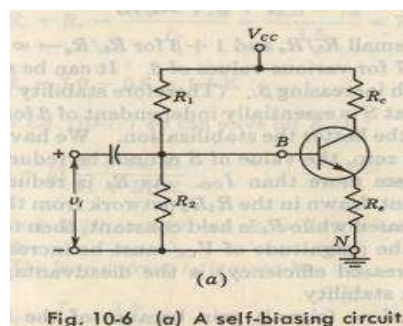**Q.2** Assume that a silicon transistor with  $\beta = 50$ ,  $V_{BE} = 0.6\text{ V}$ ,  $V_{CC} = 22.5\text{ V}$ , and  $R_c = 5.6\text{ K}$  is used in Fig. given below. It is desired to establish a Q-point at  $V_{CE} = 12\text{ V}$ ,  $I_C = 1.5\text{ mA}$ , and a stability factor  $S \leq 3$ . then determine  $R_E$ ,  $R_1$  and  $R_2$



**Solution** The current in  $R_e$  is  $I_C + I_B \approx I_C$ . Hence, from the collector circuit of Fig. 10-6b, we have

$$R_e + R_c = \frac{V_{CC} - V_{CE}}{I_C} = \frac{22.5 - 12}{1.5} = 7.0 \text{ K}$$

or

$$R_e = 7.0 - 5.6 = 1.4 \text{ K}$$

From Eq. (10-17) we can solve for  $R_b/R_e$ :

$$3 = 51 \frac{1 + R_b/R_e}{51 + R_b/R_e}$$

We find  $R_b/R_e = 2.12$  and  $R_b = 2.12 \times 1.4 = 2.96 \text{ K}$ . If  $R_b < 2.96 \text{ K}$ , then  $S < 3$ .

The base current  $I_B$  is given by

$$I_B \approx \frac{I_C}{\beta} = \frac{1.5}{50} \text{ mA} = 30 \mu\text{A}$$

We can solve for  $R_1$  and  $R_2$  from Eqs. (10-14). We find

$$R_1 = R_b \frac{V_{CC}}{V} \quad R_2 = \frac{R_1 V}{V_{CC} - V} \quad (10-18)$$

From Eqs. (10-15) and (10-18) we obtain

$$V = (0.030)(2.96) + 0.6 + (0.030 + 1.5)(1.4) = 2.83 \text{ V}$$

$$R_1 = \frac{2.96 \times 22.5}{2.83} = 23.6 \text{ K}$$

$$R_2 = \frac{23.6 \times 2.83}{22.5 - 2.83} = 3.38 \text{ K}$$

**Q3.** For a voltage divider biasing circuit with  $V_{BE} = 0.65\text{ V}$ ,  $V_{CC} = 22.5\text{ V}$ , and  $R_C = 5.6\text{ K}$ ,  $R_E = 1\text{ K}$ ,  $R_1 = 90\text{ K}$ ,  $R_2 = 10\text{ K}$ .

- (i) Determine Q-point if  $\beta = 55$ .
- (ii) Determine Q-point if  $\beta = 200$
- (iii) Compare the results of both (i) and (ii) and give the comment on insensitivity of self-bias circuit to the variation in  $\beta$

$$V_{th} = V_{CC} \times \frac{R_2}{R_1 + R_2} = 22.5 \times \frac{10}{100} = 2.25\text{ V}, \quad R_{th} = 10 \times \frac{90}{100} = 9\text{ K}$$

Applying KVL in Base Emitter loop

$$V_{th} - V_{BE} = I_B * R_{th} + (I_B + I_C) * R_E,$$

$$2.25 - 0.65 = I_B * (1 + 9) + I_C * 1,$$

Applying KVL in Collector Emitter loop

$$V_{CC} - V_{CE} = I_B * 1 + (I_C) * 6.6,$$

We know that  $I_B = \frac{I_C}{\beta}$ ,

After substituting all values, we got  **$I_B = 24.8\text{ }\mu\text{A}$ ,  $I_C = 1.36\text{ mA}$ , and  $V_{CE} = 13.5\text{ V}$**

(ii) For second part we have to find all values with  $\beta = 200$

$$\mathbf{I_B = 7.6\text{ }\mu\text{A}, I_C = 1.52\text{ mA, and } V_{CE} = 12.5\text{ V}}$$


**(ii) Comparing these values with that of previous values shows that  $V_{CE}$  changes by only 1 volt as beta changes from 55 to 200. This demonstrate the relative in-sensitivity of the self-bias circuit to variation in beta**

**Q4.** Determine the stability factor (S and S'') for collector to base biasing circuit.

**Q5.** Derive an expression of stabilization factor ( $S'' = \frac{\Delta I_C}{\Delta \beta}$ ) in terms of stabilization factor (S).

Q4 →

## Collector to Base Biasing

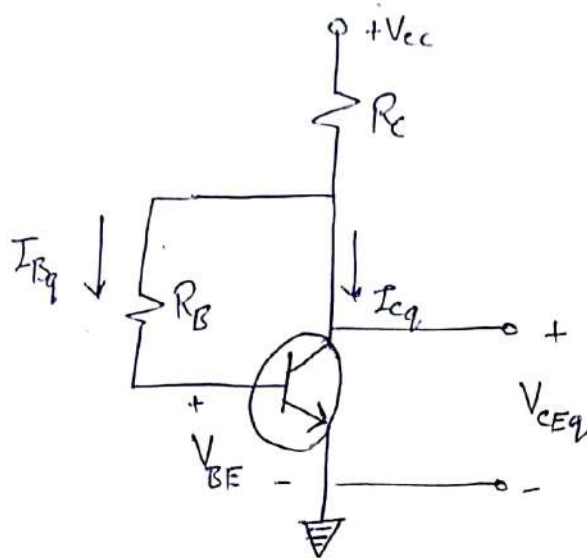

Applying KVL in Base-emitter loop through  $V_{CC}$

$$V_{CC} - V_{BE} = (I_B + I_C) R_C + I_B R_B \quad \text{--- (1)}$$

$$\Rightarrow I_{Bq} = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta)R_C} \quad \because I_C \approx \beta I_B$$

$$I_{Cq} = \beta I_{Bq}$$

$$V_{CEq} = V_{CC} - (I_B + I_C) R_C$$

Differentiate eqn. (1) w.r.t  $I_C$

$$R_B \frac{\partial I_B}{\partial I_C} + R_C \frac{\partial I_B}{\partial I_C} + R_C = 0$$


$$\boxed{\frac{\partial I_B}{\partial I_C} = \frac{-R_C}{R_B + R_C}}$$

$$\text{Stability factor } S = \frac{1+\beta}{1 - \frac{\partial I_B}{\partial I_C} \beta} = \frac{1+\beta}{1 + \beta \frac{R_C}{R_B + R_C}}$$



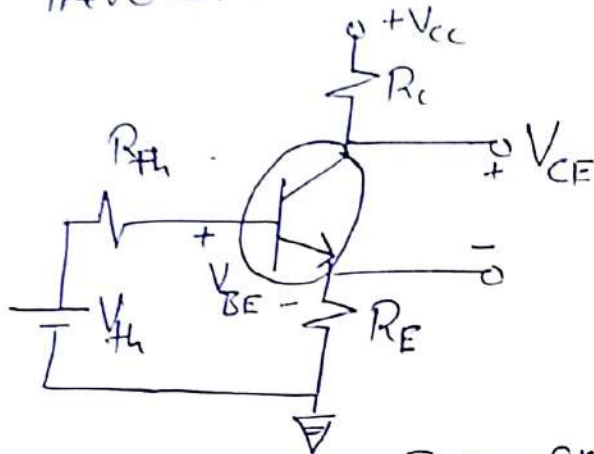Q5 Solution of  $s'' = \frac{\partial I_c}{\partial \beta}$

For a voltage divider circuit; after applying Thevenin theorem the resultant ckt is



$$V_{TH} = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

Applying KVL in Base-emitter loop

$$V_{TH} - V_{BE} = I_B R_{TH} + (I_B + I_C) R_E \quad \text{--- (1)}$$

We know that  $I_C = \beta I_B + (1 + \beta) I_{CO}$  --- (2)

Substitute the value of  $I_B$  from eqn. (2) into (1)

$$I_B = \frac{I_C}{\beta} - \frac{I_{CO}(1 + \beta)}{\beta}$$

$$V_{TH} - V_{BE} = I_B (R_{TH} + R_E) + I_C R_E \quad \text{--- (3)}$$

$$V_{TH} - V_{BE} = \frac{(R_{TH} + R_E) I_C}{\beta} - \frac{(R_{TH} + R_E)(1 + \beta) I_{CO}}{\beta} + I_C R_E$$

Differentiate w.r.t  $\beta$  ( $I_{CO}$  &  $V_{BE}$   $\neq$  constant)

$$\frac{\partial (V_{TH} - V_{BE})}{\partial \beta} = 0 = \frac{\partial I_C}{\partial \beta} \frac{(R_{TH} + R_E)}{\beta} - \frac{I_C (R_{TH} + R_E)}{\beta^2} + \frac{I_{CO} (R_{TH} + R_E)}{\beta^2} + \frac{\partial I_C}{\partial \beta} R_E \quad \text{--- (3)}$$

$$\Rightarrow \left( \frac{R_{TH} + R_E}{B^2} \right) [I_C - I_{C0}] = \frac{\partial I_C}{\partial B} \left[ \frac{R_{TH} + R_E}{B} + R_E \right] \quad (4)$$

Since  $I_C \gg I_{C0}$ ;  $I_{C0}$  can be neglected.

$$\Rightarrow \left( \frac{R_{TH} + R_E}{B^2} \right) I_C = \beta'' \left[ \frac{R_{TH} + R_E (1+B)}{B} \right] \quad (5)$$

$$\Rightarrow \beta'' = \frac{I_C (R_{TH} + R_E)}{(B) (R_{TH} + R_E (1+B))} \quad (6)$$

$$\Rightarrow \beta'' = \frac{I_C}{B} \frac{(1 + R_{TH}/R_E)}{(1+B + R_{TH}/R_E)} \quad (7)$$

$$\therefore \beta = \frac{(1+B) (1 + R_{TH}/R_E)}{1+B + R_{TH}/R_E}$$

$$\Rightarrow \beta'' = \frac{I_C \beta}{(B) (1+B)} \quad (8)$$

Change in collector current due to change in  $B$  is

$$\Delta I_C = \beta'' \Delta B = \frac{I_C \beta}{B(1+B)} (\Delta B) \quad (9)$$

where  $\Delta B = B_2 - B_1$

From eq. (9), it is not clear whether to use  $B_1, B_2$  or some average value of  $B$ .

This problem may be avoided if  $\beta''$  is obtained by taking finite differences rather than by evaluating a derivative.

$$\beta'' = \frac{\Delta I_C}{\Delta B} = \frac{I_{C2} - I_{C1}}{B_2 - B_1}$$

Now consider eqn. (3) again

$$I_B(R_{TH} + R_E) + I_C R_E = V_{TH} - V_{BE} \quad \text{--- (3)}$$

$$\therefore I_B \approx \frac{I_C}{\beta} \quad \text{neglecting } I_{C0}$$

$$\Rightarrow I_C = \frac{\beta (V_{TH} - V_{BE})}{R_{TH} + (1 + \beta) R_E} \quad \text{--- (4)}$$

$$\Rightarrow \text{at } \underline{\underline{\beta_1 = \beta_1}} \quad I_C = I_{C1} = \frac{\beta_1 (V_{TH} - V_{BE})}{R_{TH} + (1 + \beta_1) R_E} \quad \text{--- (5)}$$

$$\text{at } \beta = \beta_2 \quad I_C = I_{C2} = \frac{\beta_2 (V_{TH} - V_{BE})}{R_{TH} + (1 + \beta_2) R_E} \quad \text{--- (6)}$$

$$\Rightarrow \frac{I_{C2}}{I_{C1}} = \frac{\beta_2}{\beta_1} \left[ \frac{R_{TH} + R_E (1 + \beta_1)}{R_{TH} + R_E (1 + \beta_2)} \right] \quad \text{--- (7)}$$

$$\Rightarrow \frac{I_{C2}}{I_{C1}} - 1 = \left( \frac{\beta_2}{\beta_1} - 1 \right) \left[ \frac{R_{TH} + R_E}{R_{TH} + R_E (1 + \beta_2)} \right] \quad \text{--- (8)}$$

$$\Rightarrow s'' = \frac{I_{C2} - I_{C1}}{\beta_2 - \beta_1} = \frac{(I_{C1}) (R_{TH} + R_E)}{\beta_1 [R_{TH} + R_E (1 + \beta_2)]} \quad \text{--- (9)}$$

$$\Rightarrow \boxed{s'' = \frac{I_{C1} s_2}{\beta_1 (1 + \beta_2)}} \quad \text{--- (10)}$$

This is the final expression